

SEPIC Converter Calculations For Fixed Output Voltage

Junaid PV (<http://junaid.site>)

August 15, 2019

1 Introduction

This document makes calculation to design a SEPIC converter. Calculations are based on “[AN-1484 Designing A SEPIC Converter](#)” by Dongbing Zhang from *Texas Instruments*.

2 Parameters

- Minimum input voltage, $V_{IN(min)} = 7 \text{ V}$
- Maximum input voltage, $V_{IN(max)} = 24 \text{ V}$
- Output voltage, $V_{OUT} = 14.2 \text{ V}$
- Maximum out current, $I_{OUT} = 4 \text{ A}$
- Switching frequency, $f_{sw} = 100.0 \text{ kHz}$

2.1 MOSFET (IRLZ44N)

- Static Drain-to-Source On-Resistance, $R_{DS(ON)} = 22.0 \text{ m}\Omega$
- Gate-to-Drain (“Miller”) Charge, $Q_{GD} = 25.0 \text{ nC}$
- Gate drive current, $I_G = 350.0 \text{ mA}$

2.2 Diode (1N5825)

- Forward voltage drop of diode, $V_D = 0.38 \text{ V}$

3 Duty Cycle

Maximum duty cycle is given by

$$D_{max} = \frac{V_{OUT} + V_D}{V_{IN(min)} + V_{OUT} + V_D}$$

then, $D_{max} = 67.56\%$

Minimum duty cycle is given by

$$D_{min} = \frac{V_{OUT} + V_D}{V_{IN(min)} + V_{OUT} + V_D}$$

then, $D_{min} = 37.79\%$

4 Inductor Selection

Ripple current is given by

$$\Delta I_L = I_{IN} \times 40\% = I_{OUT} \times \frac{V_{OUT}}{V_{IN(min)}} \times 40\%$$

The inductor value is given by:

$$L1 = L2 = L = \frac{V_{IN(min)}}{\Delta I_L \times f_{SW}} \times D_{max}$$

then, $L1 = L2 = L = 14.6 \mu\text{H}$

For coupled inductor, value will be $2L = 29.1 \mu\text{H}$

The peak current in the inductor is given by:

$$I_{L1(peak)} = I_{OUT} \times \frac{V_{OUT} + V_D}{V_{IN(min)}} \times \left(1 + \frac{40\%}{2}\right)$$

$$I_{L2(peak)} = I_{OUT} \times \left(1 + \frac{40\%}{2}\right)$$

5 Power MOSFET Selection

Peak switch current is given by:

$$I_{Q1(peak)} = I_{L1(peak)} + I_{L2(peak)}$$

then, $I_{Q1(peak)} = 14.8 \text{ A}$

The RMS current through the switch is given by:

$$I_{Q1(rms)} = I_{OUT} \sqrt{\frac{(V_{OUT} + V_{IN(min)} + V_D) \times (V_{OUT} + V_D)}{V_{IN(min)}^2}}$$

then, $I_{Q1(rms)} = 10.14 \text{ A}$

The MOSFET power dissipation is given by:

$$P_{Q1} = I_{Q1(rms)}^2 \times R_{DS(ON)} \times D_{max} + (V_{IN(min)} + V_{OUT}) \times I_{Q1(peak)} \times \frac{Q_{GD} \times f_{SW}}{I_G}$$

then, $P_{Q1} = 10.14 \text{ Watts}$

6 Output Diode Selection

Peak current is 14.8 A.

The minimum peak reverse voltage the diode must withstand is:

$$V_{RD1} = V_{IN(max)} + V_{OUT(max)}$$

then, $V_{RD1} = 38.2$ V

Power dissipation by diode is given by:

$$P_{D1} = V_D \times I_{OUT}$$

then, $P_{D1} = 1.52$ Watts

7 SEPIC Coupling Capacitor Selection

The selection of SEPIC capacitor, C_s , depends on the RMS current, which is given by:

$$I_{C_s(rms)} = I_{OUT} \times \sqrt{\frac{V_{OUT} + V_D}{V_{IN(min)}}}$$

then, $I_{C_s(rms)} = 5.77$ A

The peak-to-peak ripple voltage on C_s (assuming no ESR):

$$\Delta V_{C_s} = \frac{I_{OUT} \times D_{max}}{C_s \times f_{SW}}$$

then, $C_s = 270.3$ μ F

8 Output Capacitor Selection

The RMS current in the output capacitor is:

$$I_{C_{out}(rms)} = I_{OUT} \times \sqrt{\frac{V_{OUT} + V_D}{V_{IN(min)}}}$$

then, $I_{C_{out}(rms)} = 5.77$ A

Output capacitance,

$$C_{out} \geq \frac{I_{OUT} \times D}{V_{ripple} \times 0.5 \times f_{SW}}$$

then, $C_{out} = 540.5$ μ F

9 Input Capacitor Selection

The RMS current in the input capacitor is given by:

$$I_{C_{in}(rms)} = \frac{\Delta I_L}{\sqrt{12}}$$

then, $I_{C_{in}(rms)} = 3.2$ A